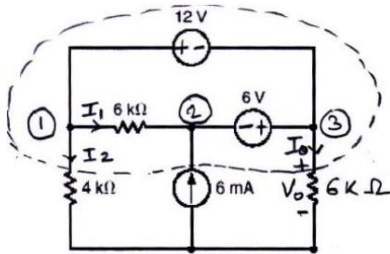


1)



KCL at supernode : $6\text{mA} = I_2 + I_o$
 $\frac{V_1}{4\text{k}} + \frac{V_3}{6\text{k}} = 6\text{mA}$

$$3V_1 + 2V_3 = 72$$


$$V_1 - V_3 = 12$$

$$\begin{aligned} 3V_1 + 2V_3 &= 72 \\ V_1 - V_3 &= 12 \end{aligned}$$

$$V_1 = 19.2 \text{ V}$$

$$V_3 = 7.2 \text{ V}$$

$$V_o = V_3 = 7.2 \text{ V}$$

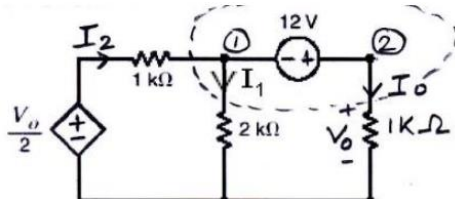

KCL at supernode : $I_2 = I_1 + I_o$

$$\frac{\frac{V_o}{2} - V_1}{1\text{k}} = \frac{V_1}{2\text{k}} + \frac{V_2}{1\text{k}}$$

$$V_o = V_2$$

$$\frac{\frac{V_2}{2} - V_1}{1\text{k}} = \frac{V_1}{2\text{k}} + \frac{V_2}{1\text{k}}$$

$$V_2 - 2V_1 = V_1 + 2V_2$$

$$\boxed{3V_1 + V_2 = 0}$$

$$V_2 - V_1 = 12$$

$$\boxed{-V_1 + V_2 = 12}$$

$$3V_1 + V_2 = 0$$

$$-V_1 + V_2 = 12$$


$$V_1 = -3V$$

$$V_2 = 9V$$

$$V_0 = V_2 = 9V$$

$$V_0 = 9V$$

2)

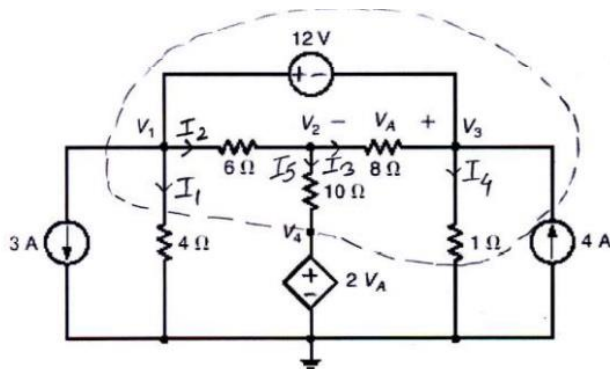

$$\text{KCL at (2): } I_2 = I_5 + I_3$$

$$\frac{V_1 - V_2}{6} = \frac{V_2 - V_4}{10} + \frac{V_2 - V_3}{8}$$

$$5V_1 - 5V_2 = 3V_2 - 3V_4 + 3.75V_2 - 3.75V_3$$

$$5V_1 - 11.75V_2 + 3.75V_3 + 3V_4 = 0$$

KCL at supernode: $3 + I_1 + I_5 + I_4 = 4$

$$\frac{V_1}{4} + \frac{V_2 - V_4}{10} + \frac{V_3}{1} = 1$$

$$5V_1 + 2V_2 - 2V_4 + 20V_3 = 20$$

$$5V_1 + 2V_2 + 20V_3 - 2V_4 = 20$$

$$V_1 - V_3 = 12$$

$$V_4 = 2V_A$$

$$V_A = V_3 - V_2$$

$$V_4 = 2(V_3 - V_2)$$

$$-2V_2 + 2V_3 - V_4 = 0$$

$$5V_1 - 11.75V_2 + 3.75V_3 + 3V_4 = 0$$

$$5V_1 + 2V_2 + 20V_3 - 2V_4 = 20$$

$$V_1 + 0V_2 - V_3 + 0V_4 = 12$$

$$0V_1 - 2V_2 + 2V_3 - V_4 = 0$$


$$V_1 = 9.68 \text{ V}$$

$$V_2 = 1.45 \text{ V}$$

$$V_3 = -2.32 \text{ V}$$

$$V_4 = -7.54 \text{ V}$$

3)

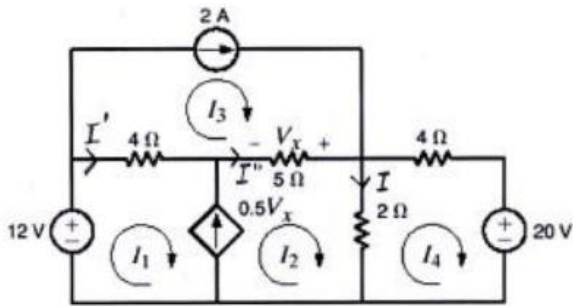

$$\text{KCL: } I_1 = I' + I_3$$

$$I' = I_1 - I_3$$

$$\text{KCL: } I + I_4 = I_2$$

$$I = I_2 - I_4$$

$$\text{KCL: } I'' + I_3 = I + I_4$$

$$I'' = -I_3 + I_4 + I_2 - I_4$$

$$I'' = I_2 - I_3$$

$$\text{KCL: } I_2 = 0.5V_x + I_1$$

$$-I_1 + I_2 - 0.5V_x = 0$$

$$V_x = -I''(5) = -5(I_2 - I_3)$$

$$V_x = -5I_2 + 5I_3$$

$$-I_1 + I_2 - 0.5(-5I_2 + 5I_3) = 0$$

$$\boxed{-I_1 + 3.5I_2 - 2.5I_3 = 0}$$

$$I_3 = 2A$$

$$\text{KVL: } 4I_4 + 20 + 2(-I) = 0$$

$$4I_4 - 2(I_2 - I_4) = -20$$

$$\boxed{-2I_2 + 6I_4 = -20}$$

$$\text{KVL: } 12 = 4I' + 5I'' + 4I_4 + 20$$

$$4(I_1 - I_3) + 5(I_2 - I_3) + 4I_4 = -8$$

$$4I_1 + 5I_2 - 9I_3 + 4I_4 = -8$$

$$\boxed{4I_1 + 5I_2 + 4I_4 = 10}$$

$$-I_1 + 3.5I_2 - 2.5I_3 = 0$$

$$-2I_2 + 6I_4 = -20$$

$$4I_1 + 5I_2 + 4I_4 = 10$$

$$I_3 = 2A$$

$$-I_1 + 3.5I_2 = 5$$

$$-2I_2 + 6I_4 = -20$$


$$4I_1 + 5I_2 + 4I_4 = 10$$

$$I_1 = 2.46A$$

$$I_2 = 2.13A$$

$$I_4 = -2.62A$$

4)

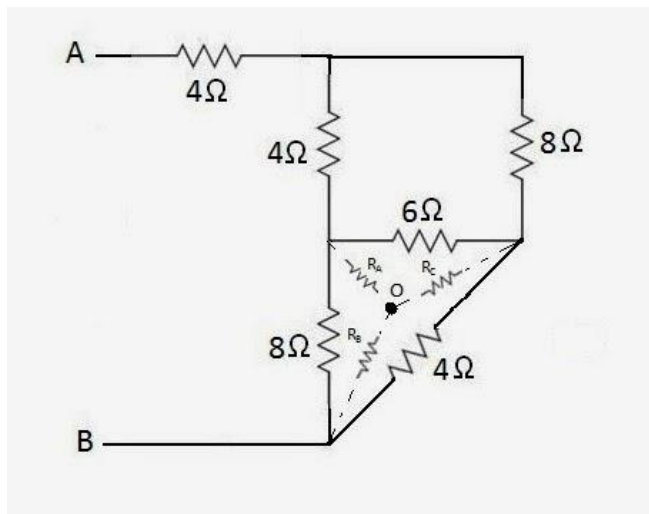

$$R_A = \frac{8 \cdot 6}{8 + 6 + 4}$$


$$R_A = 2.66\Omega$$


$$R_C = \frac{6 \cdot 4}{8 + 6 + 4}$$

$$R_C = 1.33\Omega$$

$$R_B = \frac{8 \cdot 4}{8 + 6 + 4}$$


$$R_B = 1.77\Omega$$

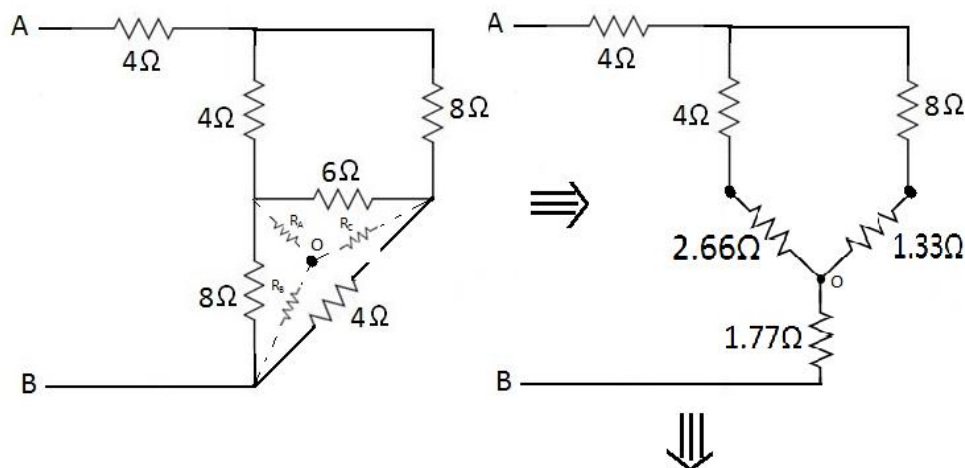

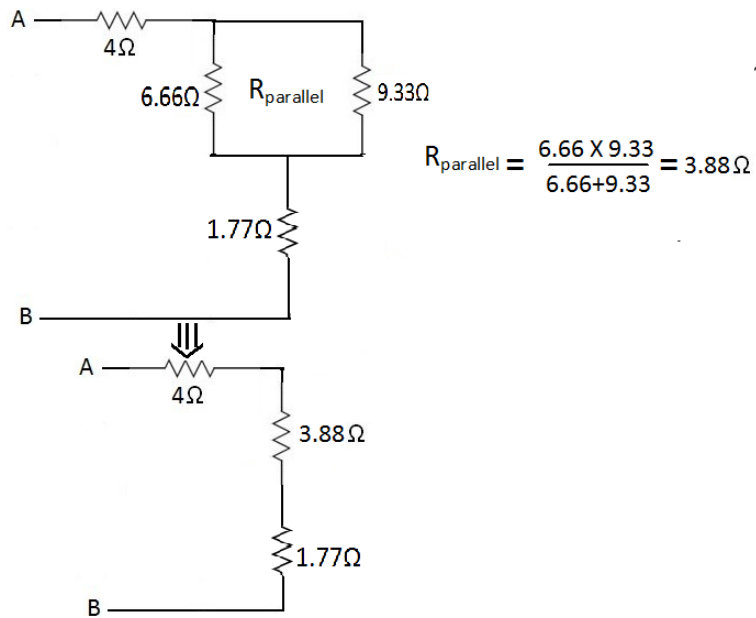

So, $R_{AB} (R_{\text{equivalent}}) = R_1 + R_2 + R_3 = 4\Omega + 3.88\Omega + 1.77\Omega = 9.65\Omega$

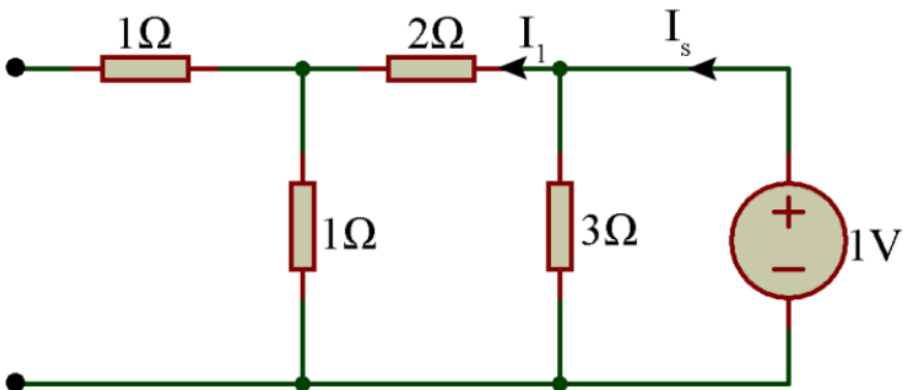5) Kill the current source and calculate I_1 ;




$$I_s = \frac{1V}{[(1 + 2) || 3]\Omega} = \frac{1}{1.5}A$$

$$I_1 = I_s \frac{3}{3 + 2 + 1} = \frac{1}{1.2} \times \frac{3}{6} = \frac{1}{3}A$$

(by current division)

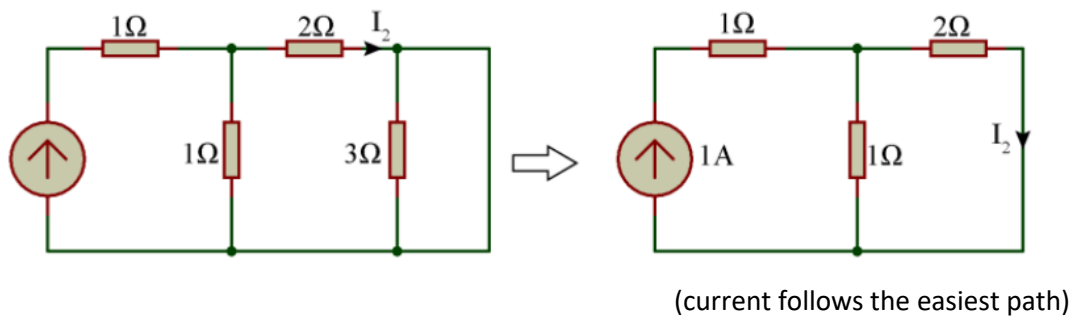Now, kill the voltage source and calculate I_2 ;




$$I_2 = 1 \times \frac{1}{1+2} = \frac{1}{3} A$$

(by current divider)

$$I = (I_1 - I_2) = \frac{1}{3} - \frac{1}{3} = 0$$

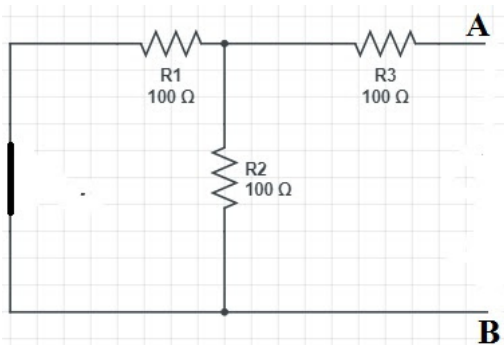
6) Step 1: Remove the load and kill the voltage source;



So, resistance across A and B (R_{eq}) is;

$$R_{eq} = R_1 \parallel R_2 + R_3 = 150 \text{ ohms.}$$

Step 2: Calculate V_{oc} across A and B;

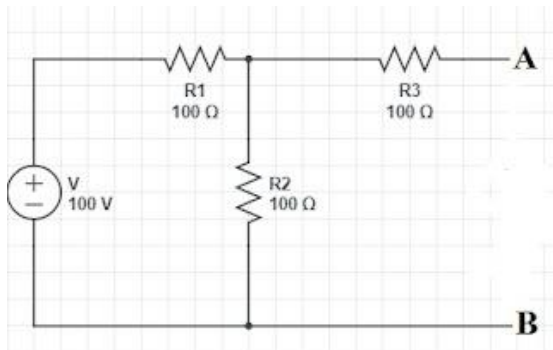


(Voltage divider)

$$V_{th} = \frac{V R_2}{R_1 + R_2}$$

$$V_{th} = \frac{100 \times 100}{100 + 100} = \frac{100 \times 100}{200} = 50$$

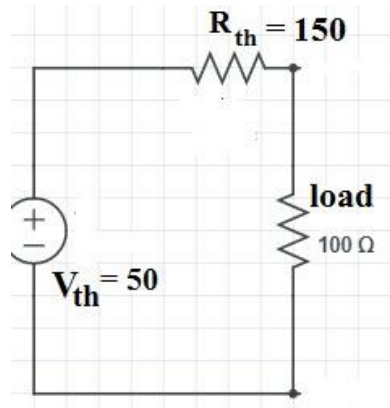Step 3: Draw the Thevenin equivalent circuit;



Find I now, which is the current flowing through the load;

$$I = \frac{V_{th}}{R_{th} + R_{load}}$$

$$I = \frac{50}{150 + 100} = \frac{50}{250} = 0.2A$$